

### HOW TO DRIVE A HIGH CURRENT RELAY GREEN-GO GPIO

To drive a relay with a drive current of more than 8mA with a GPIO output, a simple circuit with a transistor can be utilized according to the schematic below. Please note that the resistor between the power supply and pin 4/5 is dependent on the voltage of the power supply.

